

DIGITAL LOGIC

Chapter 4 part1: Combinational Logic


2023 Fall

Today's Agenda

- Recap
- Context
 - Combinational Circuits
 - Analysis of Combinational Circuits
 - Design Procedure
 - Basic Components
 - Magnitude Comparator
- Reading: Textbook, Chapter 4.1-4.4, 4.8





Recap

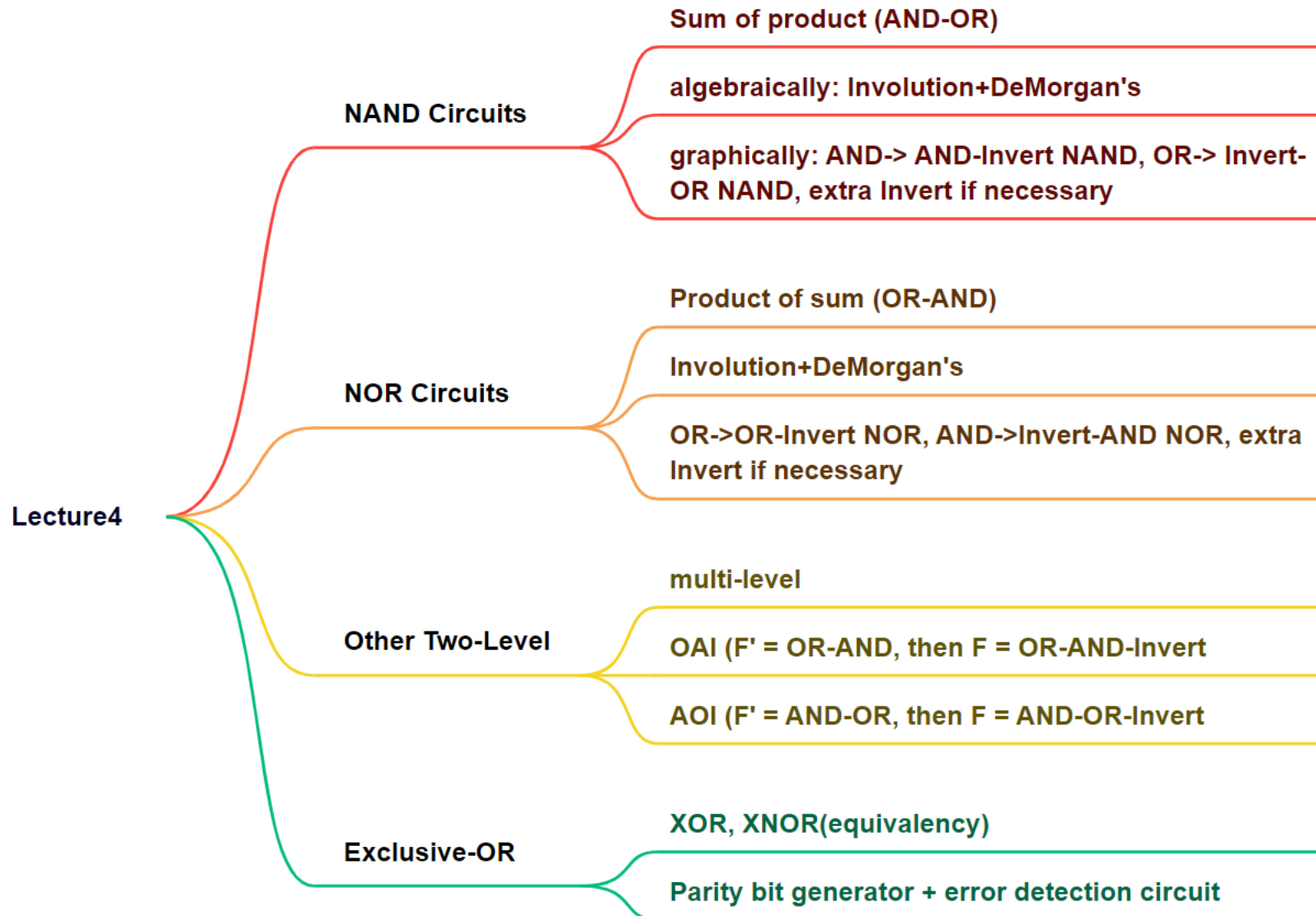



Logic Circuits for the Digital System

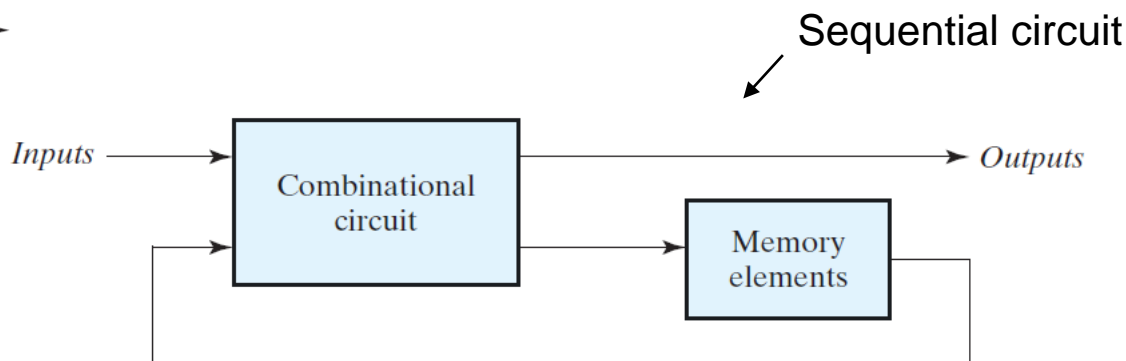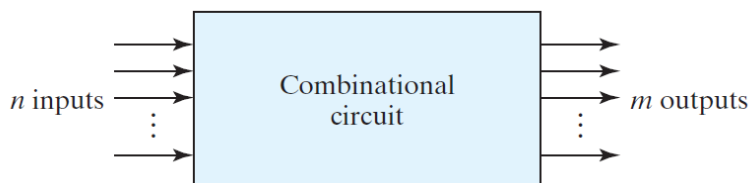- Combinational circuits
 - Logic circuits whose outputs at any time are determined directly and only from the present input combination.
- Sequential circuits (next lecture)
 - Circuits that employ memory elements + (combinational) logic gates
 - Outputs are determined from the present input combination as well as the state of the memory cells.



Combinational Logic Circuits

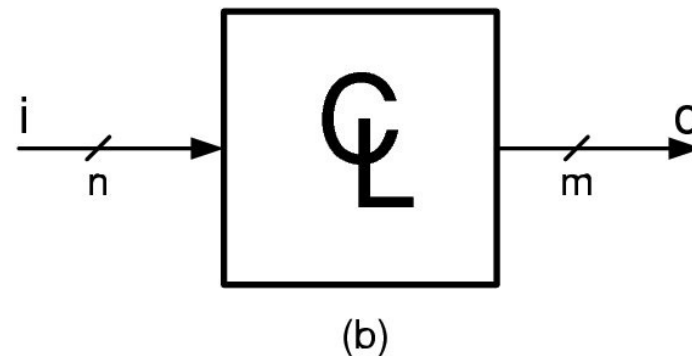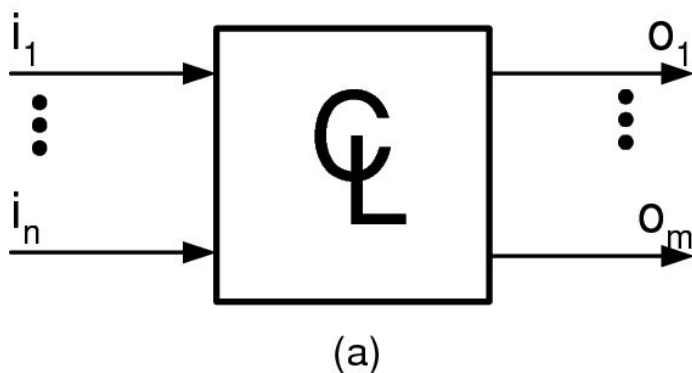- Memoryless: $o=f(i)$
 - Used for control, arithmetic, and data steering.
 - such as adders, subtractors, comparators, decoders, encoders, and multiplexers.
 - These components are available in integrated circuits as medium-scale integration (MSI) circuits



Outline

- **Analysis of Combinational Circuits**
- Design of Combinational Circuits

Analysis Procedure


- Analysis of a combinational circuit: determine the function of the circuit.
 - Given logic diagram,
 - develop a set of Boolean functions, a truth table, an optional explanation of the circuit operation.
- If a function name or an explanation is given along the circuit, just verify if the given information is correct.

Derivation of Truth Table


- For n input variables
- List all the 2^n input combinations from 0 to 2^n-1 .
- Partition the circuit into small single-output blocks and label the output of each block.
- Obtain the truth table of the blocks depending on the input variables only.
- Proceed to obtain the truth tables for other blocks that depend on previously defined truth tables.

Example

- Truth Table Approach

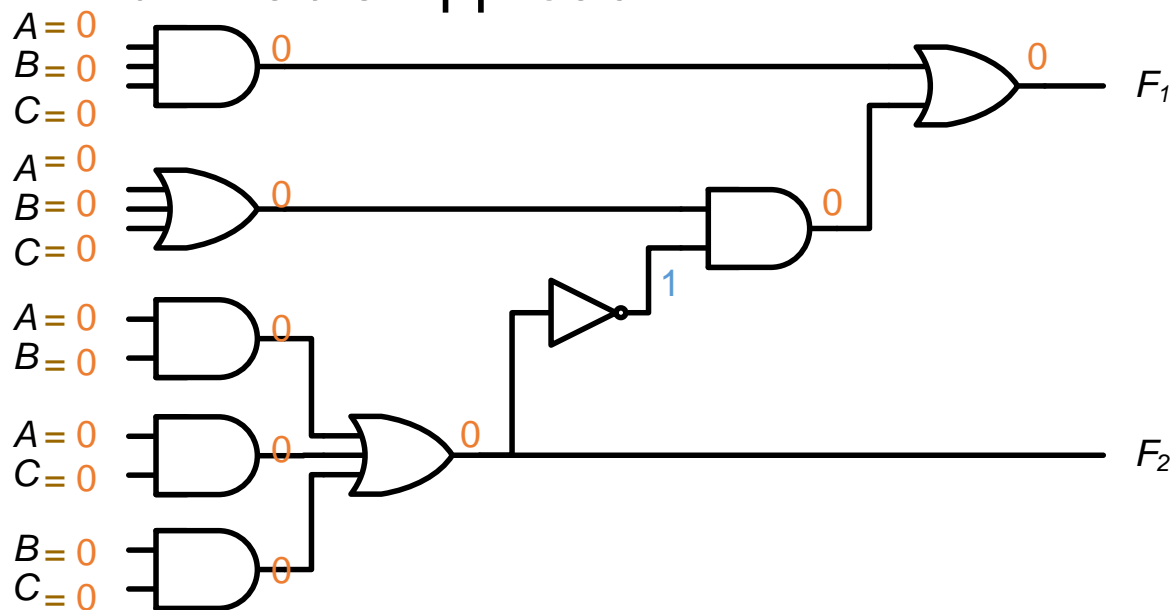
[illegible]

- Truth Table Approach

 [illegible]

Example


• Truth Table Approach

 

A	B	C	F_1	F_2
0	0	0	0 (orange)	0 (orange)
0	0	1	1 (blue)	0 (orange)
0	1	0	1 (blue)	0 (orange)

Example


• Truth Table Approach

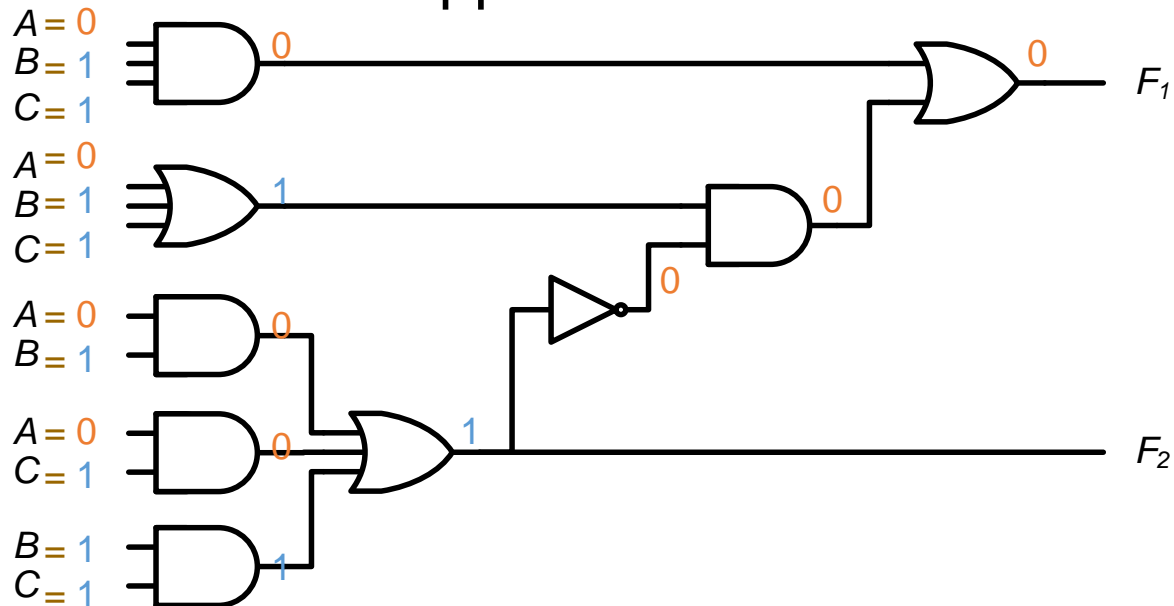

A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1

Example


• Truth Table Approach

 

A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0

Example


• Truth Table Approach

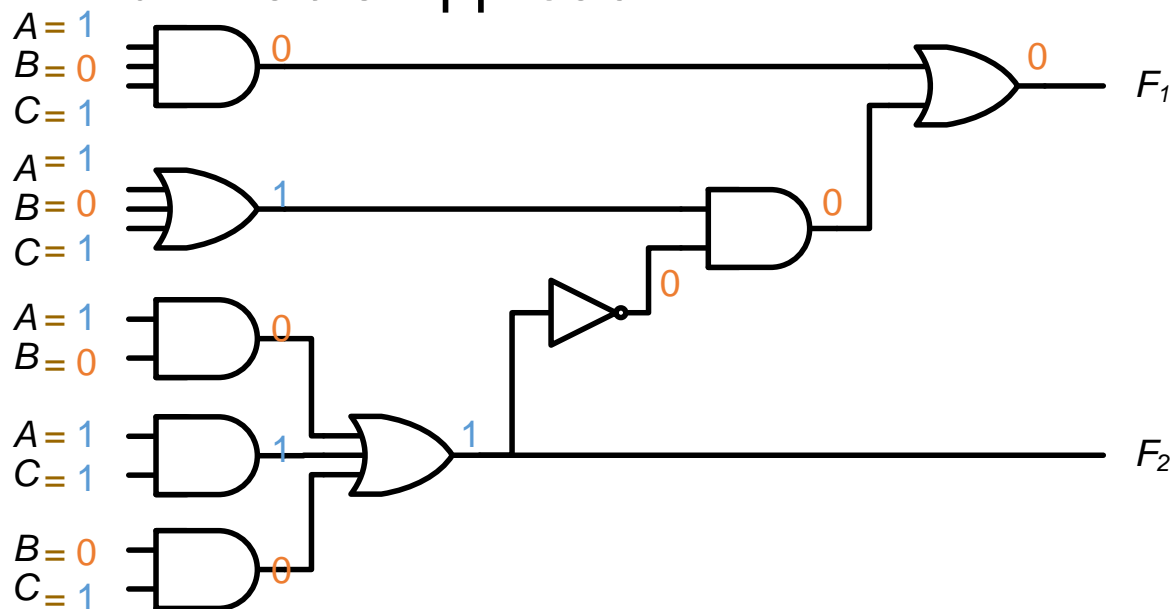

A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1

Example


- Truth Table Approach

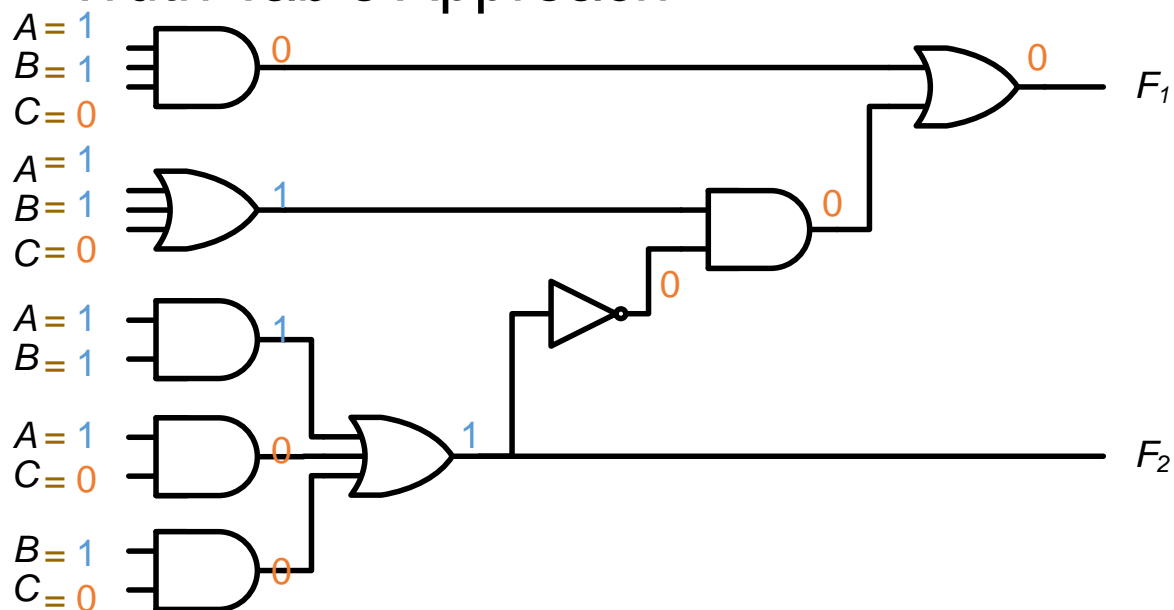

A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1

Example

- Full adder (F_1 : sum, F_2 : carry)

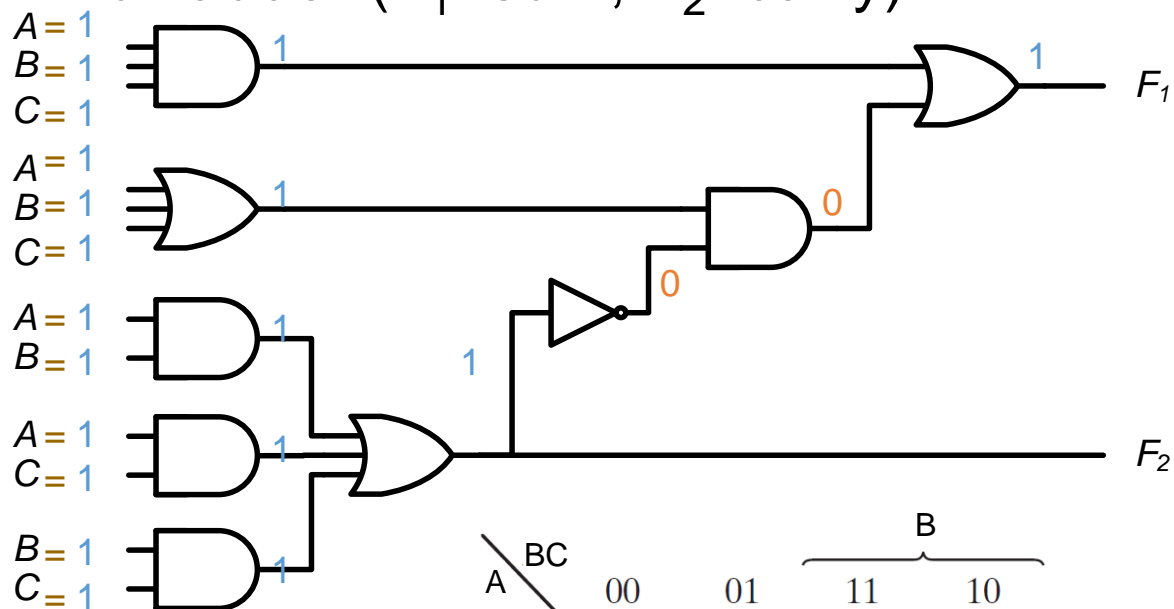

A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

A	BC			
	00	01	11	10
0	m_0 0	m_1 1	m_3 0	m_2 1
1	m_4 1	m_5 0	m_7 1	m_6 0

$$F_1 = AB'C' + A'BC' + A'B'C + ABC$$

$$= A \oplus B \oplus C$$

A	BC			
	00	01	11	10
0	m_0 0	m_1 0	m_3 1	m_2 0
1	m_4 0	m_5 1	m_7 1	m_6 1

$$F_2 = AB + AC + BC$$




Derivation of Boolean Functions

- Label all gate outputs that are functions of the input variables only. Determine the functions.
- Label all gate outputs that are functions of the input variables and previously labeled gate outputs, and find the functions.
- Repeat previous step until all the primary outputs are obtained.


Example 1

• Boolean Expression Approach

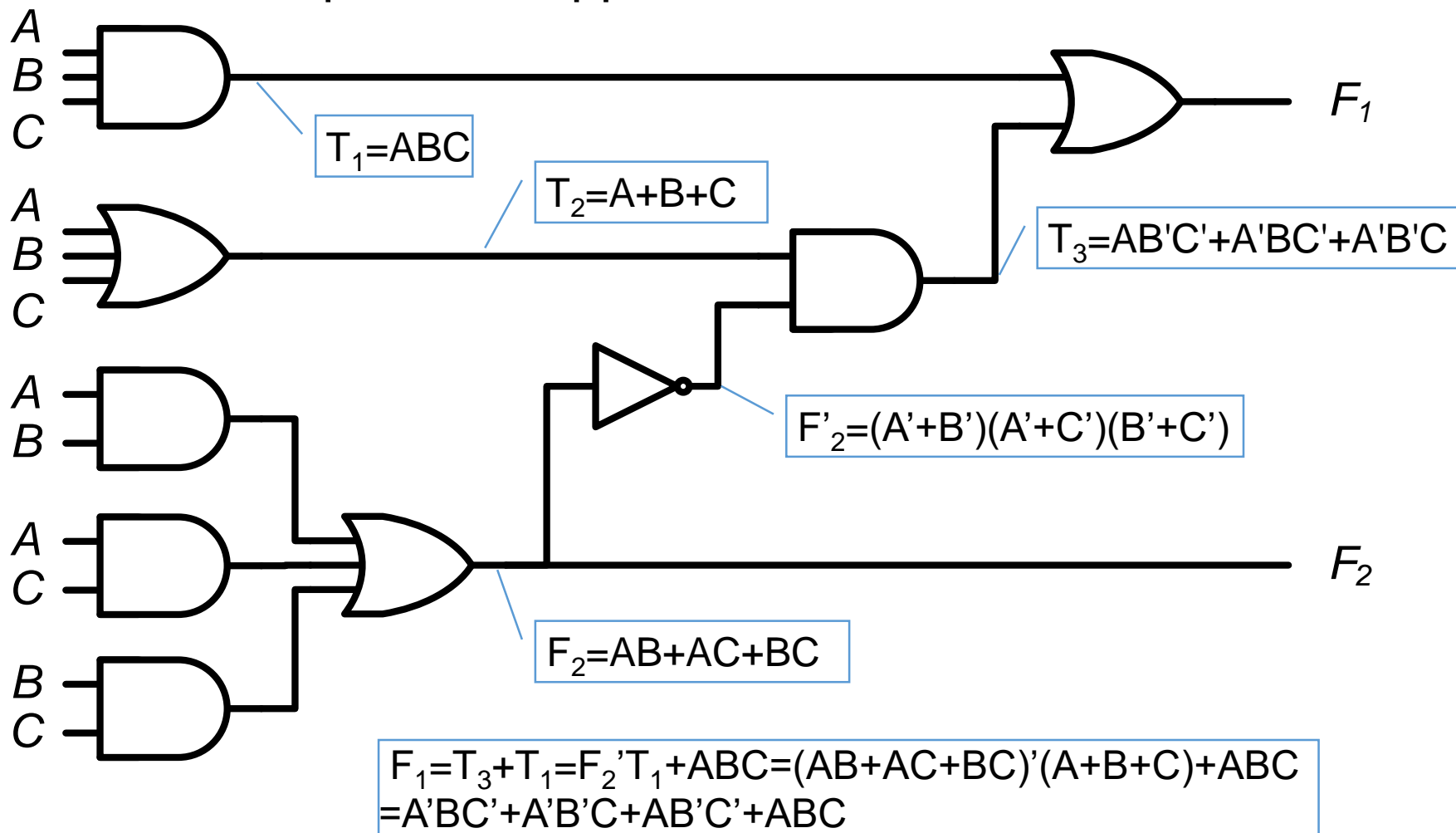

 Example 2

- Derive the Boolean expressions for T_1 through T_4 . Evaluate the outputs F_1 and F_2 as a function of the four inputs.



$$T_1 = B'C \quad T_2 = A'B \quad T_3 = A + T_1 = A + B'C$$

$$T_4 = T_2 \oplus D = T_2'D + T_2D' = (A'B)'D + A'BD' = AD + B'D + A'BD'$$

$$\begin{aligned} F_1 &= T_3 + T_4 = A + B'C + AD + B'D + A'BD' = A(1+D) + A'BD' + B'C + B'D \\ &= (A + A')(A + BD') + B'C + B'D = A + BD' + B'D + B'D \end{aligned}$$

$$F_2 = A'B + D'$$

Outline

- Analysis of Combinational Circuits
- **Design of Combinational Circuits**


Design Procedure

- Design of a combinational circuits: develop a logic circuit diagram or a set of Boolean functions.
 - From specification of the design objective
- Involves the following steps:
 1. Specification: From the specifications, determine the inputs, outputs, and their symbols.
 2. Formulation: Derive the truth table (functions) from the relationship between the inputs and outputs
 3. Optimization: Derive the simplified Boolean functions for each output.
 4. Logic diagram (optional): Draw a logic diagram for the resulting circuits using AND, OR, and inverters. (Or using required technology mapping)



 Example1: BCD-to-Excess-3 Code Converter

- Step1: Spec
 - input (ABCD)
 - output (wxyz) (MSB to LSB)
 - ABCD: 0000 ~ 1001 (0~9)
- Step2: Formulation
 - $wxyz = ABCD + 0011$



don't care

A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	x	x	x	x
1	0	1	1	x	x	x	x
1	1	0	0	x	x	x	x
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x



Example1: BCD-to-Excess-3 Code Converter

• Step3: Optimization

AB \ CD		C			
		00	01	11	10
A	00	m_0 1	m_1	m_3	m_2 1
	01	m_4 1	m_5	m_7	m_6 1
	11	m_{12} X	m_{13} X	m_{15} X	m_{14} X
	10	m_8 1	m_9	m_{11} X	m_{10} X
		D			

$z = D'$

AB \ CD		C			
		00	01	11	10
A	00	m_0 1	m_1	m_3 1	m_2
	01	m_4 1	m_5	m_7 1	m_6
	11	m_{12} X	m_{13} X	m_{15} X	m_{14} X
	10	m_8 1	m_9	m_{11} X	m_{10} X
		D			

$y = CD + C'D'$

AB \ CD		C			
		00	01	11	10
A	00	m_0	m_1 1	m_3 1	m_2 1
	01	m_4 1	m_5	m_7	m_6 1
	11	m_{12} X	m_{13} X	m_{15} X	m_{14} X
	10	m_8	m_9 1	m_{11} X	m_{10} X
		D			

$x = B'C + B'D + BC'D'$

AB \ CD		C			
		00	01	11	10
A	00	m_0	m_1	m_3	m_2
	01	m_4	m_5 1	m_7 1	m_6 1
	11	m_{12} X	m_{13} X	m_{15} X	m_{14} X
	10	m_8 1	m_9 1	m_{11} X	m_{10} X
		D			

$w = A + BC + BD$

$z = D'$
 $y = CD + C'D'$
 $x = B'C + B'D + BC'D'$
 $w = A + BC + BD$
from K-map




$z = D'$
 $y = CD + (C + D)'$
 $x = B'(C + D) + BC'D'$
 $w = A + B(C + D)$
reduce gate numbers



Example1: BCD-to-Excess-3 Code Converter

- Step4: Draw logic diagram

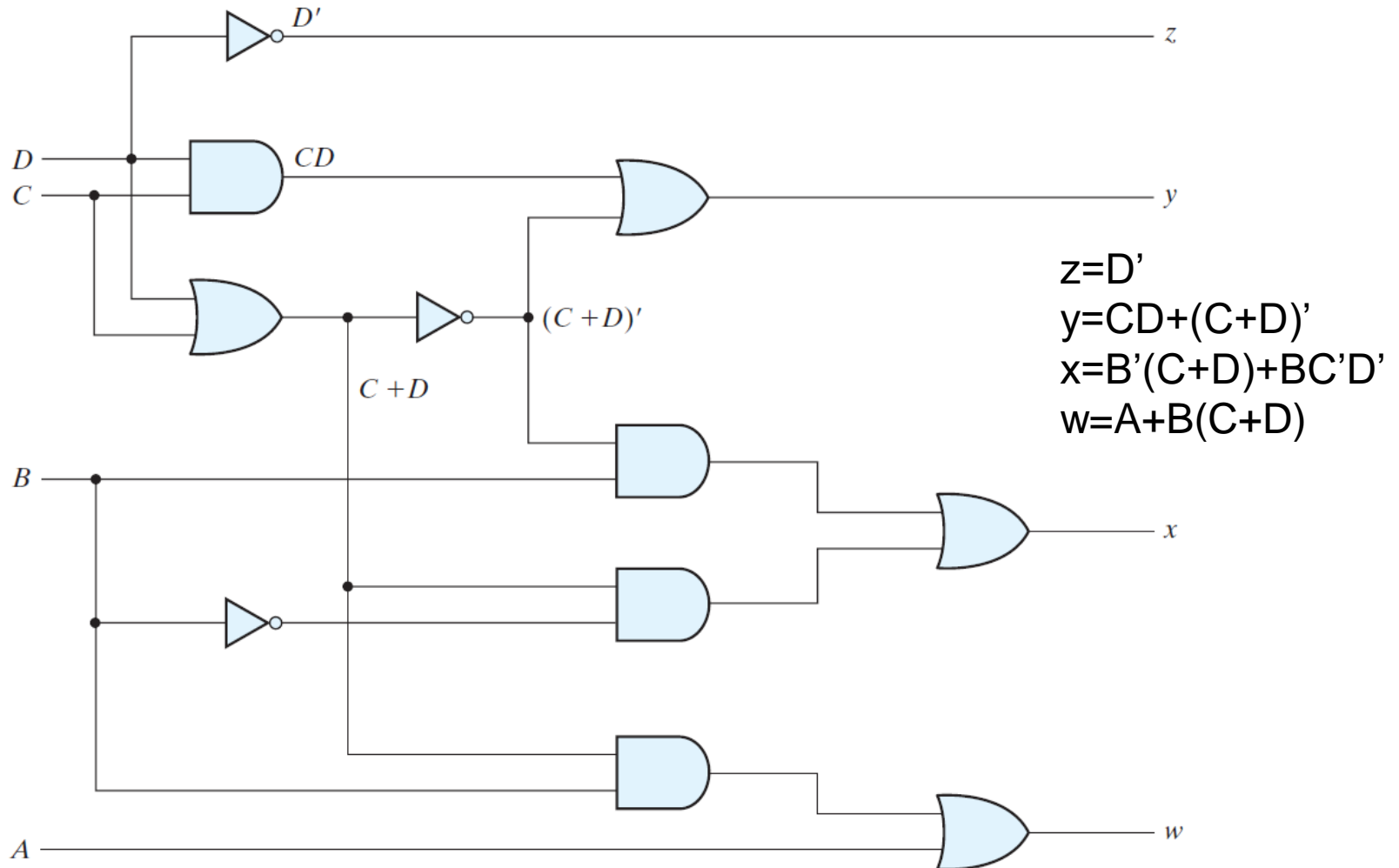

Example2: 4-bit Equality Comparator


- Step1: Spec
 - input A(3:0), B(3:0);
 - output E (1/0 for equal/unequal)
- Step2: Formulation
 - Bypass the truth table approach due to its size (8 inputs)
 - By algorithm to build a regular circuit
 - $A=A_3A_2A_1A_0$, $B=B_3B_2B_1B_0$
 - $A==B$, if $(A_3==B_3) \text{ AND } (A_2==B_2) \text{ AND } (A_1==B_1) \text{ AND } (A_0==B_0)$
 - Suppose bit equality $X_i=(A_i \oplus B_i)' = A_iB_i + A_i'B_i'$, $(A==B) = X_3X_2X_1X_0$



Hint: XNOR gate's output
Is 1 when input values
Are same

Example2: 4-bit Equality Comparator

- Step3: Optimization
 - Regularity
 - Reuse
- Step4: Draw diagram

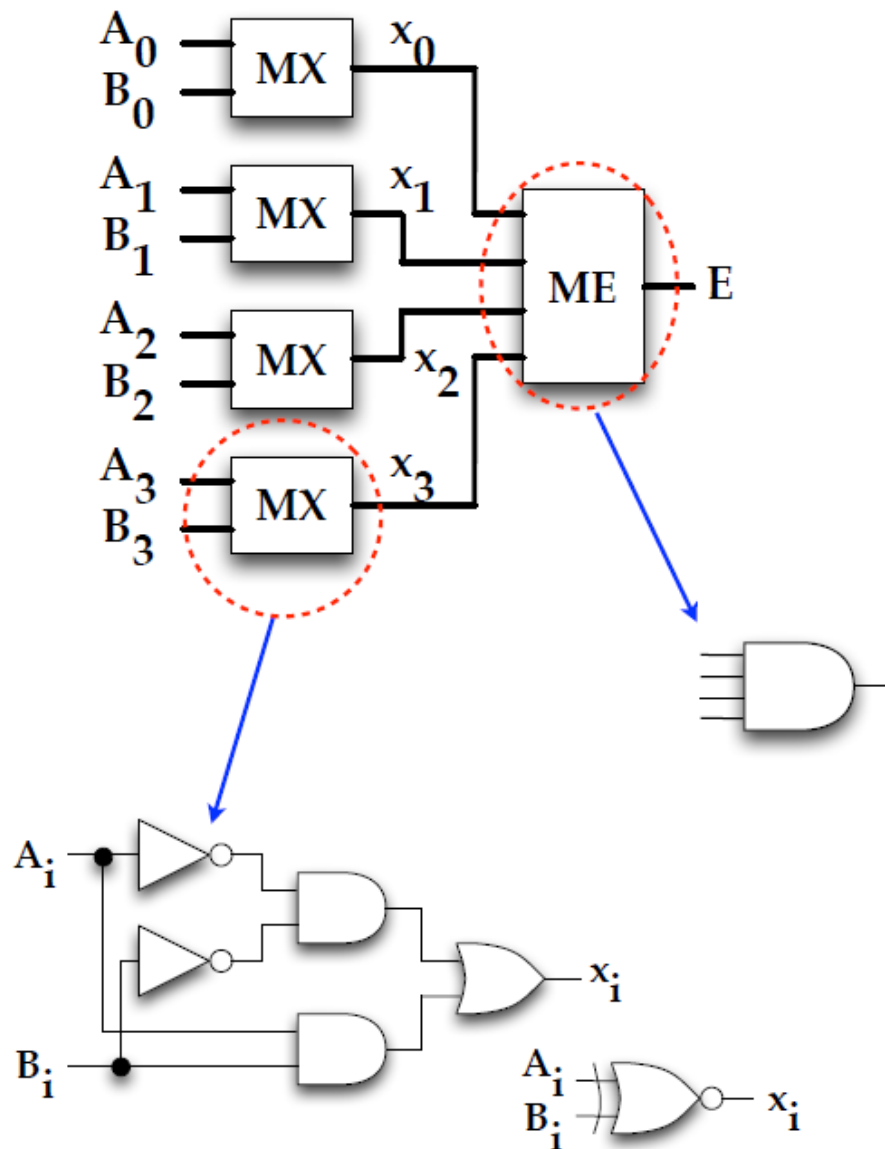

Example3: Magnitude Comparator

- Step1: Spec
 - Comparison of two numbers, three possible results ($A > B$, $A = B$, $A < B$)
- Step2: Formulation (for n-bit numbers)
 - By truth table: 2^{2n} rows \Rightarrow not practicable
 - If the truth table is too cumbersome, the regularity of comparator circuit allows deriving the function using algorithm
- Step3: Optimization
 - By algorithm to build a regular circuit
 - $A = A_3A_2A_1A_0$, $B = B_3B_2B_1B_0$
 - $A == B$, if $(A_3 == B_3) \text{ AND } (A_2 == B_2) \text{ AND } (A_1 == B_1) \text{ AND } (A_0 == B_0)$
 - equality $x_i = A_iB_i + A_i'B_i'$, $(A = B) = x_3x_2x_1x_0$
 - $(A > B) = A_3B_3' + x_3A_2B_2' + x_3x_2A_1B_1' + x_3x_2x_1A_0B_0'$
 - $(A < B) = A_3'B_3 + x_3A_2'B_2 + x_3x_2A_1'B_1 + x_3x_2x_1A_0'B_0$

Example3: Magnitude Comparator

• Step4

